




**Chapter 7: A Primer On Digital Logic** ✓

**Basic Computer Architecture**

# Outline

\*Transistors and Gates

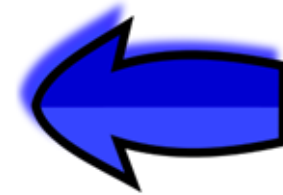

\*Combinational Logic

\* Sequential Logic

\* SRAM/ DRAM Cells

# Disclaimer: This chapter is only to



## get a high level overview ...

- \* We assume some **background** in logic gates, transistors, combinational and sequential logic
- \* The **aim** of this chapter is to only provide a [high level overview](#)
- \* For a **deeper** understanding consult any of the classic textbooks on digital logic

# Atoms and Molecules of Circuits

## The Transistor




- It is just a **switch**.
- It is either switched **on** (current can flow), or switched **off** (no current flow)

# How is a Transistor Made?


- \* It is made of **Silicon**
  - \* Silicon is a semi-conductor (neither conductor or insulator).
  - \* We can change its properties:
  - \* Add a little bit of impurities → **doping**
- \* Dope it with Group III **elements (3 valence electrons)**
  - \* Boron, Aluminum and Gallium
  - \* It is called a **p-type** semiconductor
- \* Or, dope it with Group V **elements (5 valence electrons)**
  - \* Phosphorus or Arsenic
  - \* It is called a **n-type** semiconductor

# Silicon Lattice

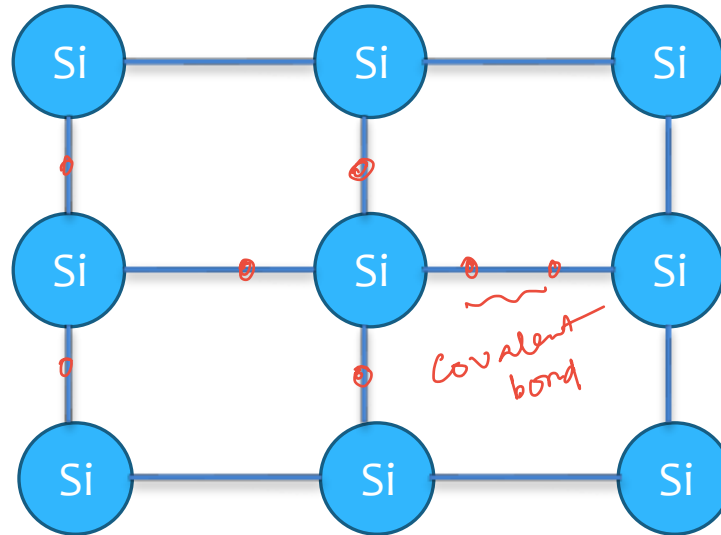


- \* This is a typical silicon lattice. Each Si atom is connected to 4 other atoms via covalent bond

# P-Type Doping

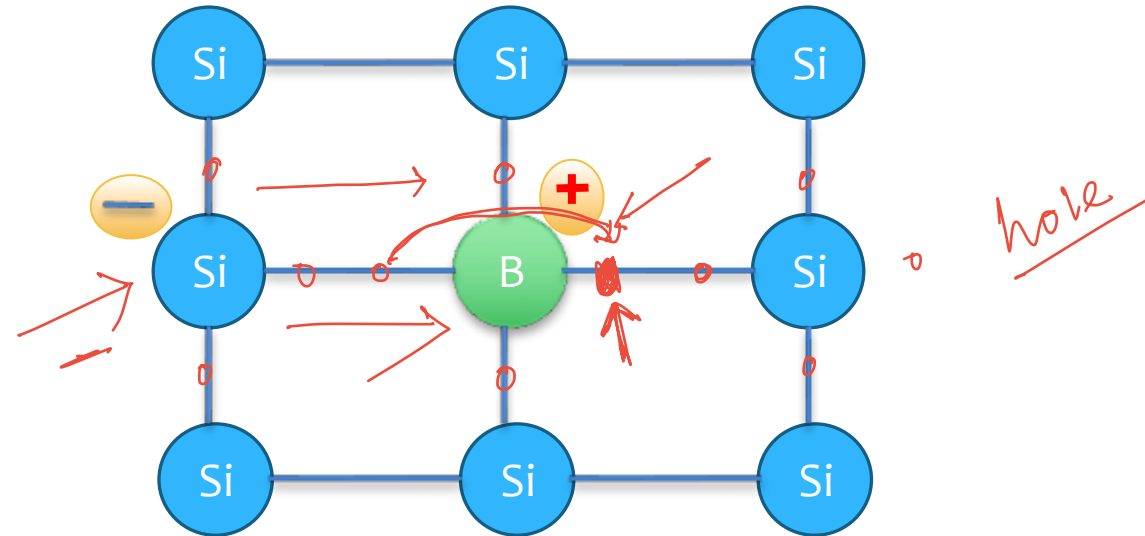


- \* If there is a Boron atom in the **lattice**. It will create bonds with the rest of the atoms.
- \* There will be one less electron (**hole**)
- \* Holes can **flow**. They are associated with +ve charge. (see the animation)

# N-Type Doping

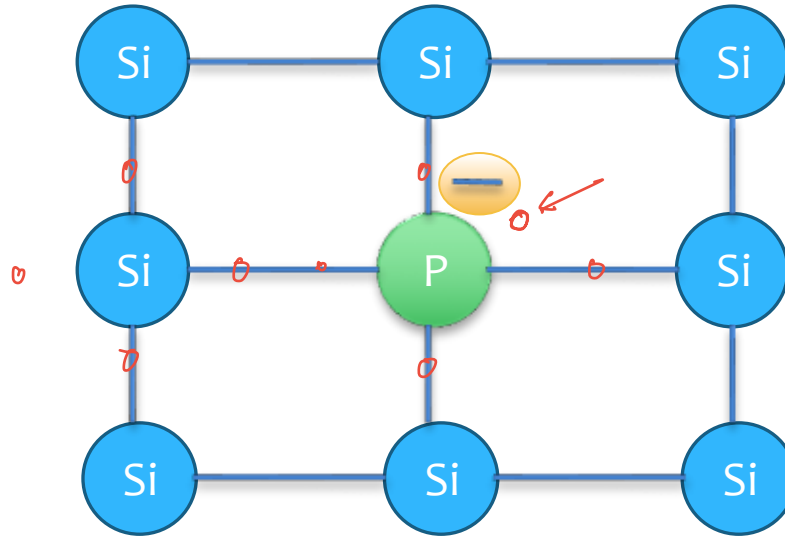

- \* If there is a Phosphorus atom in the **lattice**. It will create bonds with the rest of the atoms.
- \* There will be one more electron (**electron**)
- \* Electrons can **flow**. They are associated with -ve charge. (see the animation)


# Let us make a transistor.

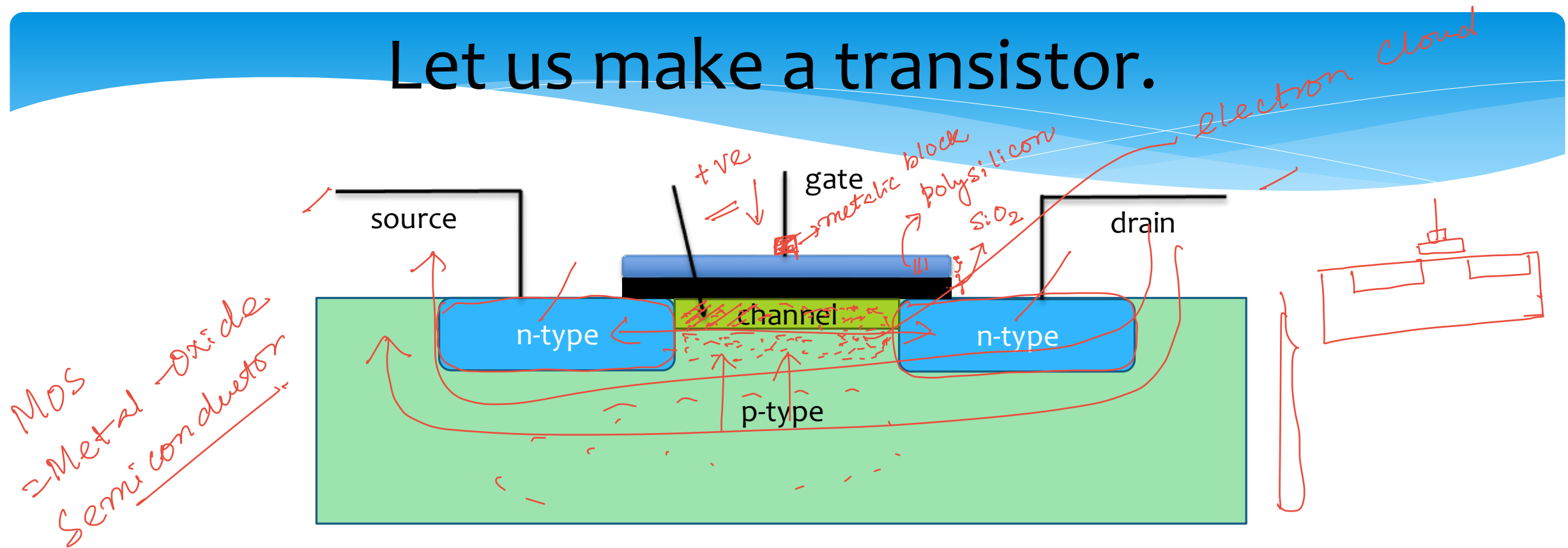

- \* NMOS transistor → Put two **n-type** wells in a **p-type** substrate
- \* Now, assume that we apply **+ve** charge to the gate.
- \* Channel → This forms because electrons move towards the positive charge. Forms a conductive layer that can conduct **current**.


# NMOS Transistor

Metal-Oxide-Semiconductor

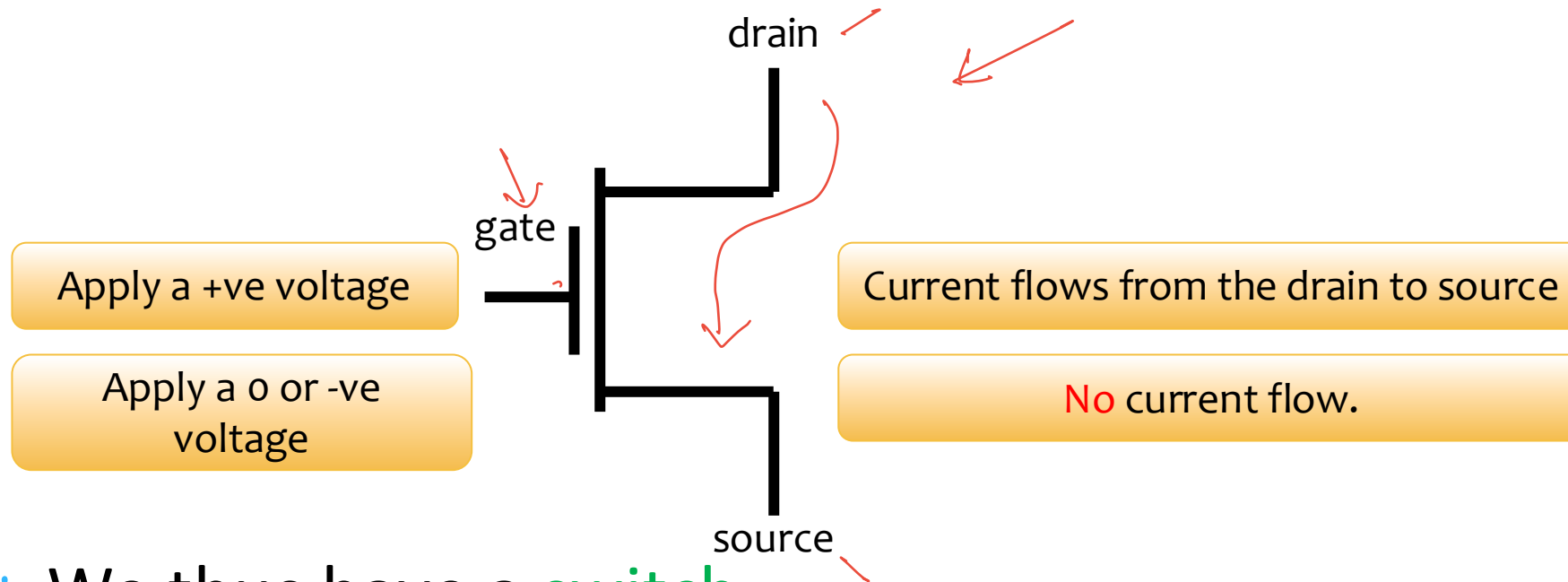


- \* We thus have a **switch**
  - \* Apply a **+ve** voltage at the gate → make the transistor conduct
  - \* Apply a **-ve** or 0 voltage at the gate → transistor is off (no current flow across it)

# PMOS Transistor

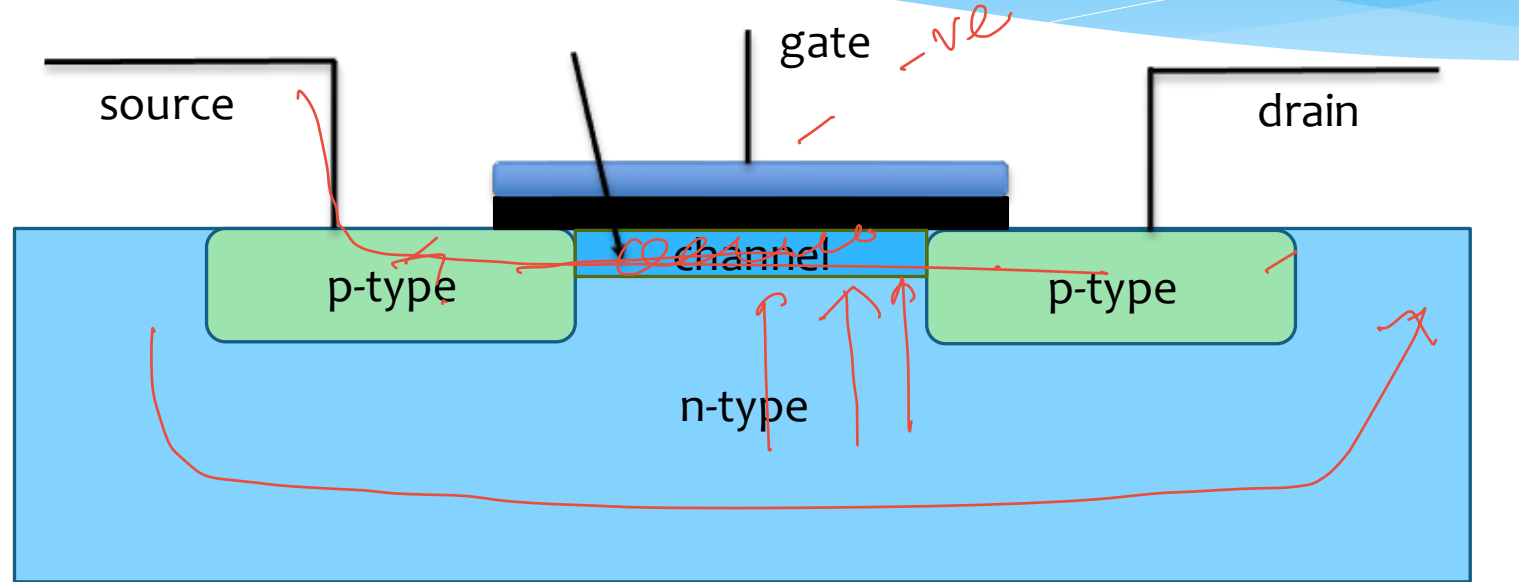

- \* PMOS transistor → Put two **p-type** wells in an **n-type** substrate
- \* Now, assume we apply **0 or -ve** charge to the gate.
- \* Channel → This forms because holes move towards the gate. This channel can conduct **current**.


# PMOS Transistor

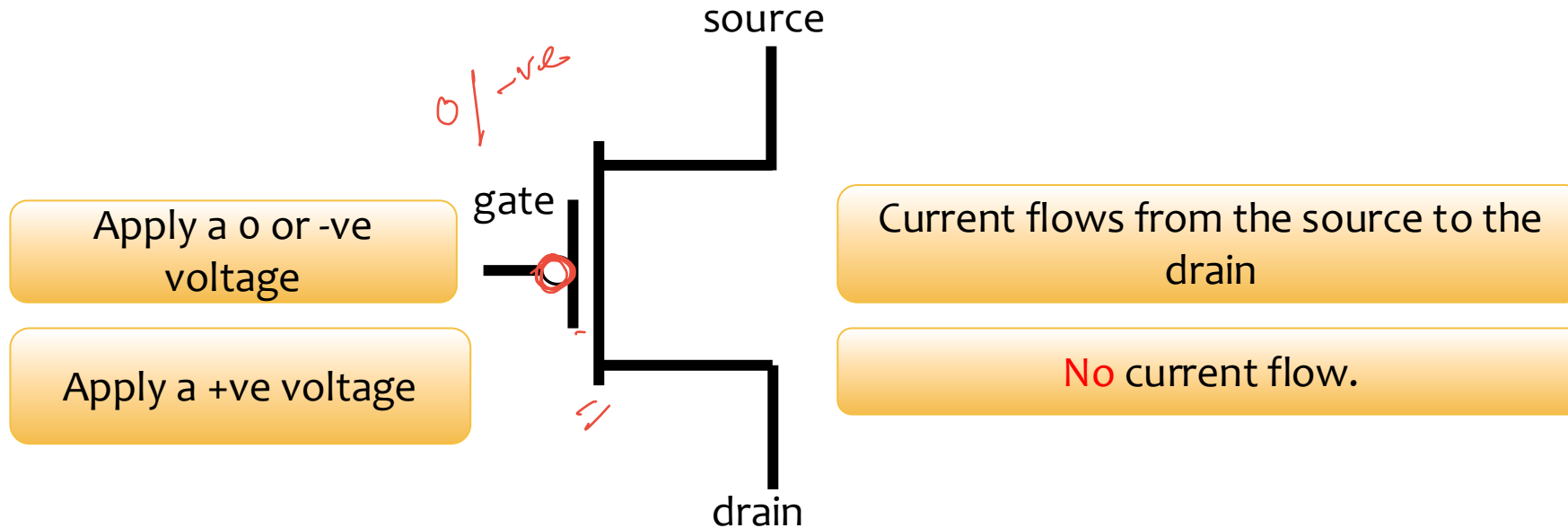

\* We thus have a **switch**

- \* Apply a **+ve** voltage at the gate → transistor is off (no current flow across it)
- \* Apply a **-ve** or 0 voltage at the gate → transistor conducts

# Let us make an inverter

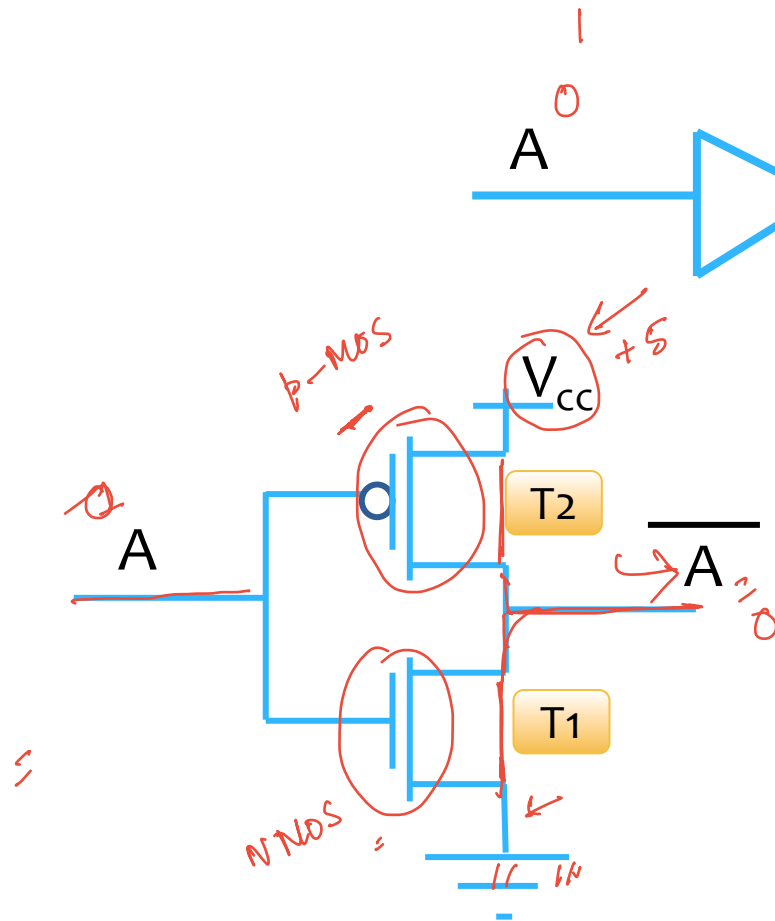


If  $A = 1$  (+ve voltage)  
T1 is on, T2 is off  
Thus, the output will be connected to the ground, and it will be a logical 0

If  $A = 0$  (0 voltage)  
T1 is off, T2 is on  
Thus, the output will be connected to the supply ( $V_{cc}$ ), and it will be a logical 1

Complementary Metal-Oxide-Semiconductor

# NOR Gate

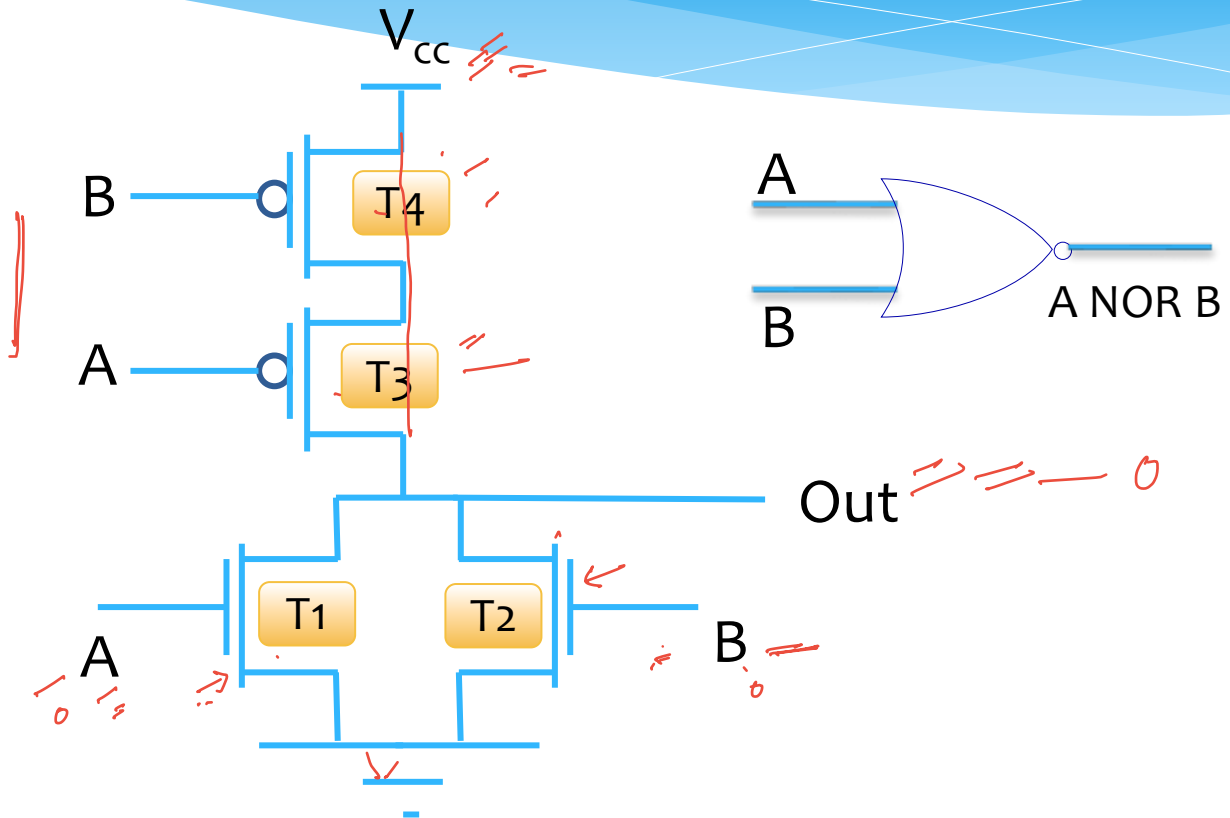


A	B	T1	T2	T3	T4	Out
0	0	off	off	on	on	1
1	0	on	off	off	on	0
0	1	off	on	on	off	0
1	1	on	on	off	off	0

NAND






A	B	O/P
0	0	1
0	1	1
1	0	0
1	1	0

# NAND Gate

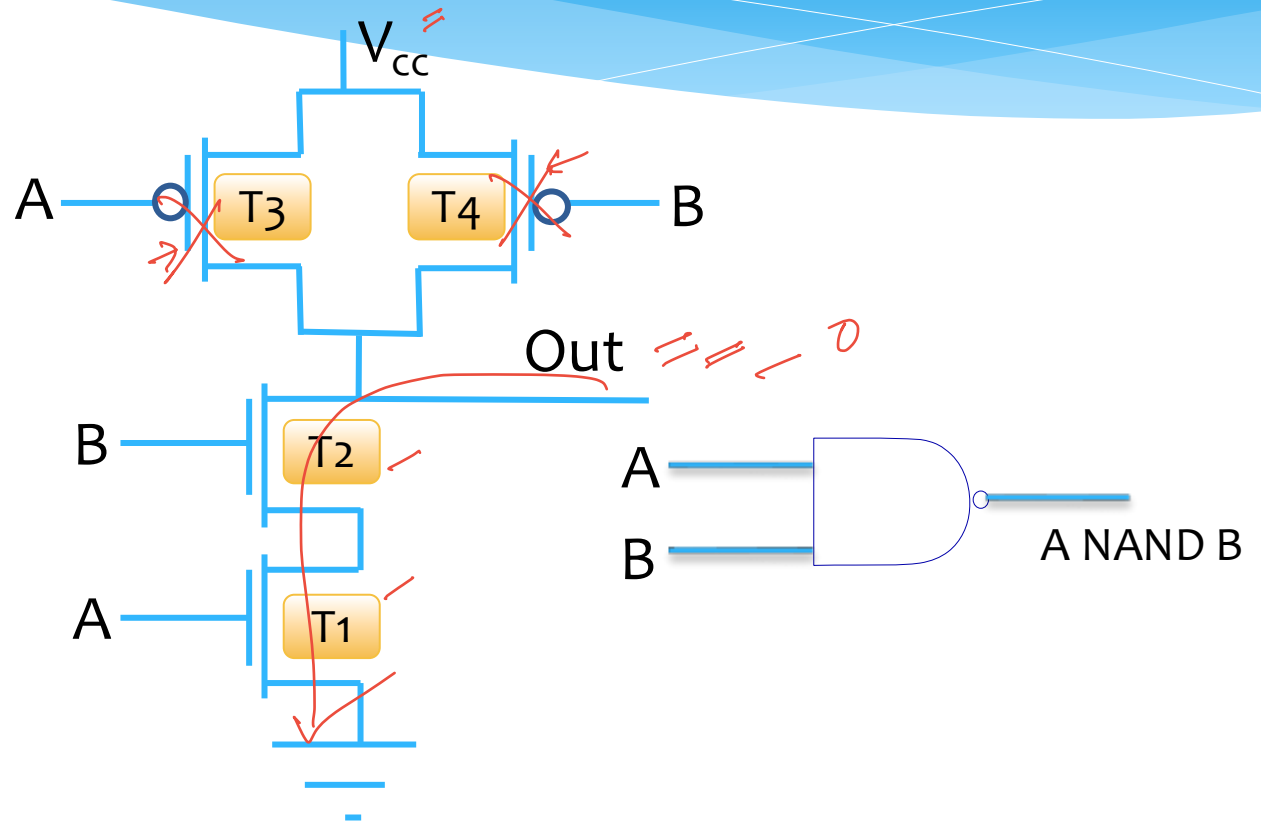


A	B	T1	T2	T3	T4	Out
0	0	off	off	on	on	1
1	0	on	off	off	on	1
0	1	off	on	on	off	1
1	1	on	on	off	off	0

# Summary of Logic Gates

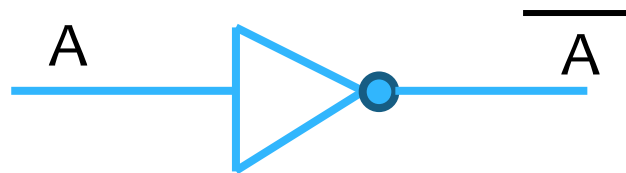    
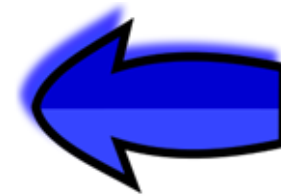
# Outline

- \* Transistors and Gates
- \* Combinational Logic
- \* Sequential Logic
- \* SRAM/ DRAM Cells








# Multiplexer

Given  $n$  **inputs**, choose one based on the **select bits**.

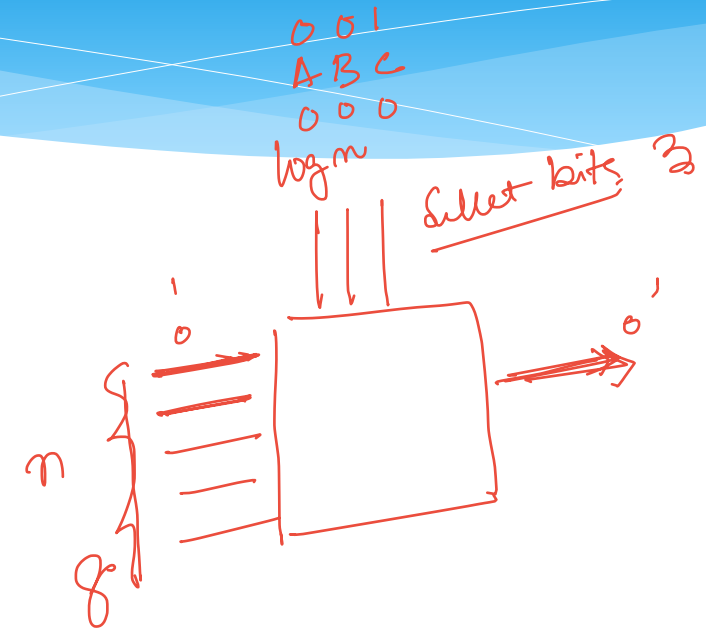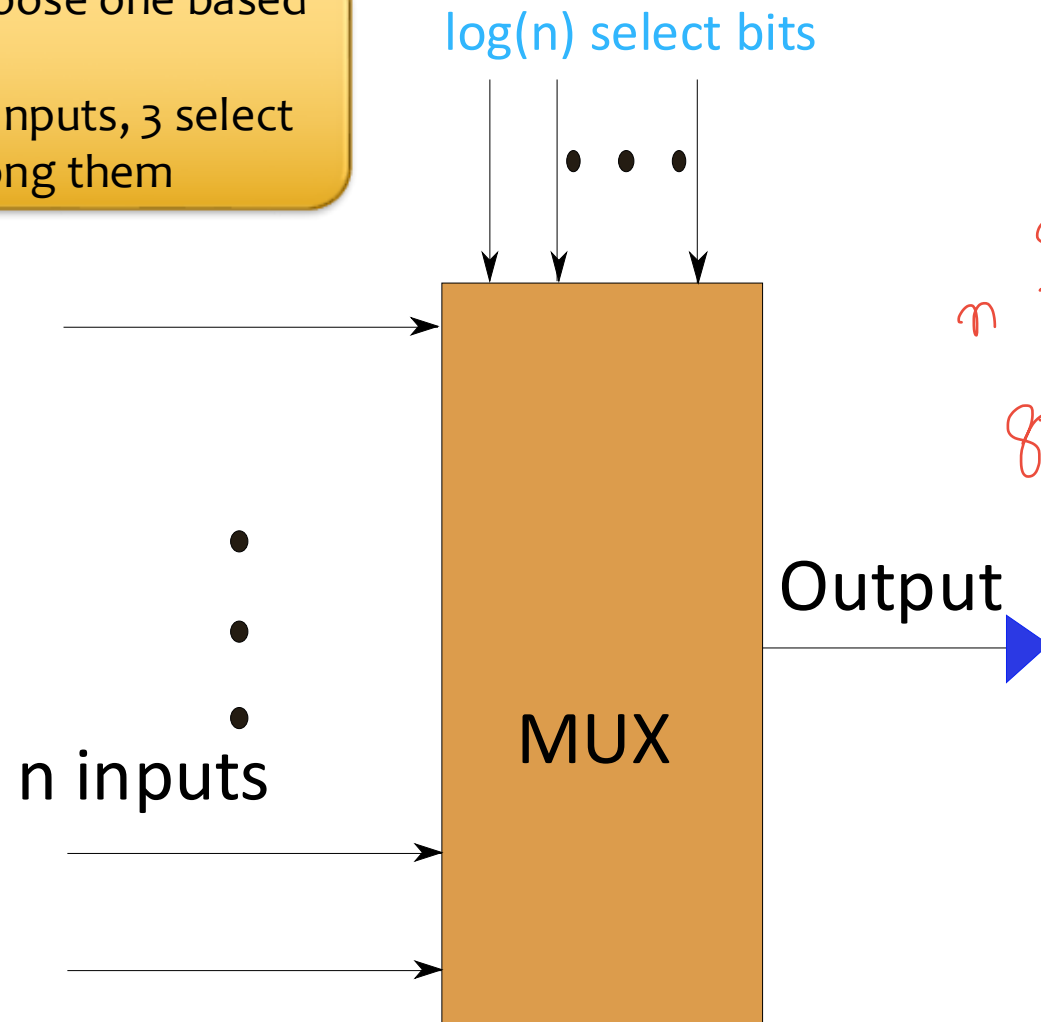Example: Given 8 inputs, 3 select bits, choose 1 among them



# Design of a Multiplexer

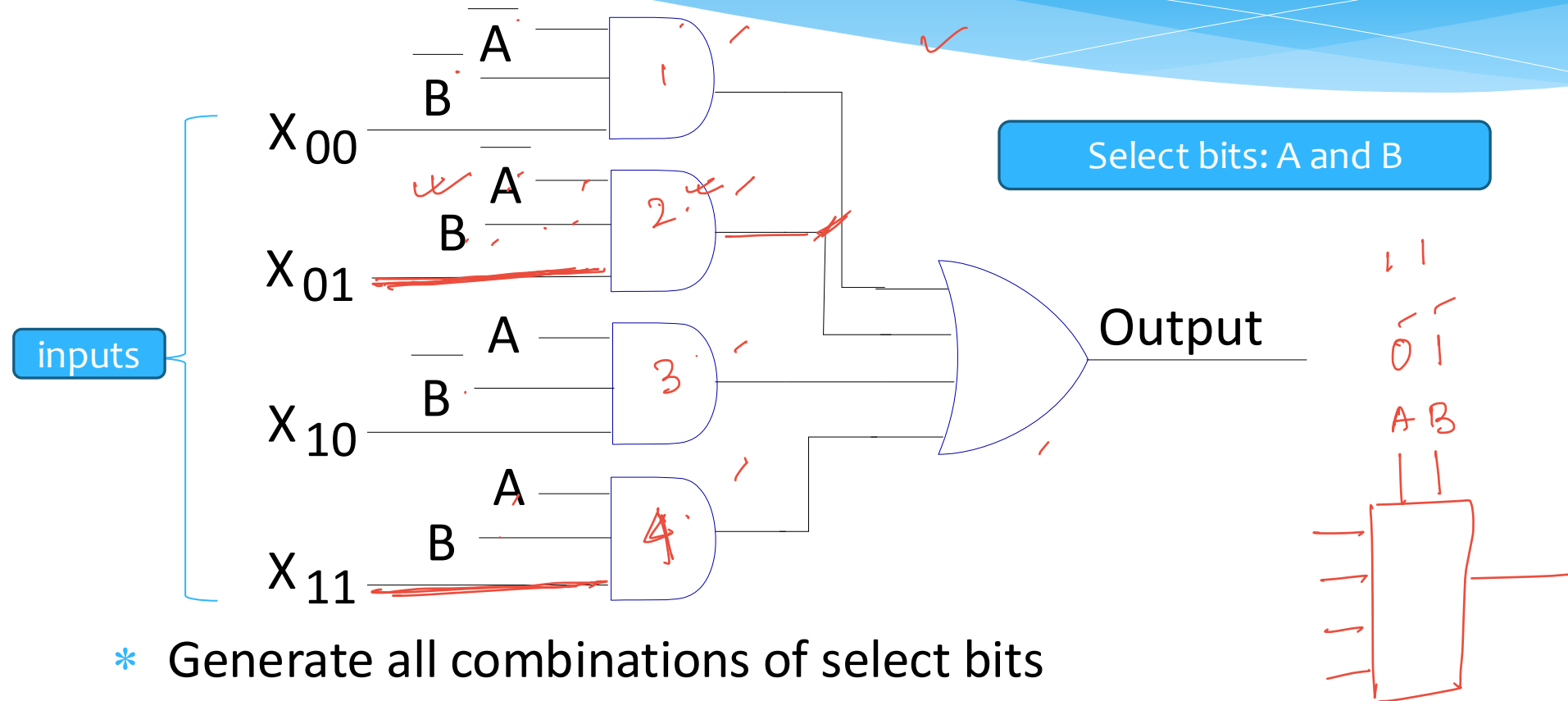

\* Generate all combinations of select bits

\*  $\bar{A} \cdot \bar{B}, A \cdot \bar{B}, \bar{A} \cdot B, A \cdot B$


\* Only one of the combinations is true.

\* For this combination the output of the AND gate is equal to the input ( $X_{AB}$ ), rest of the outputs of the AND gates are 0


\* The output is equal to  $(X_{AB} \text{ OR } 0 \text{ OR } 0 \text{ OR } 0) = X_{AB}$
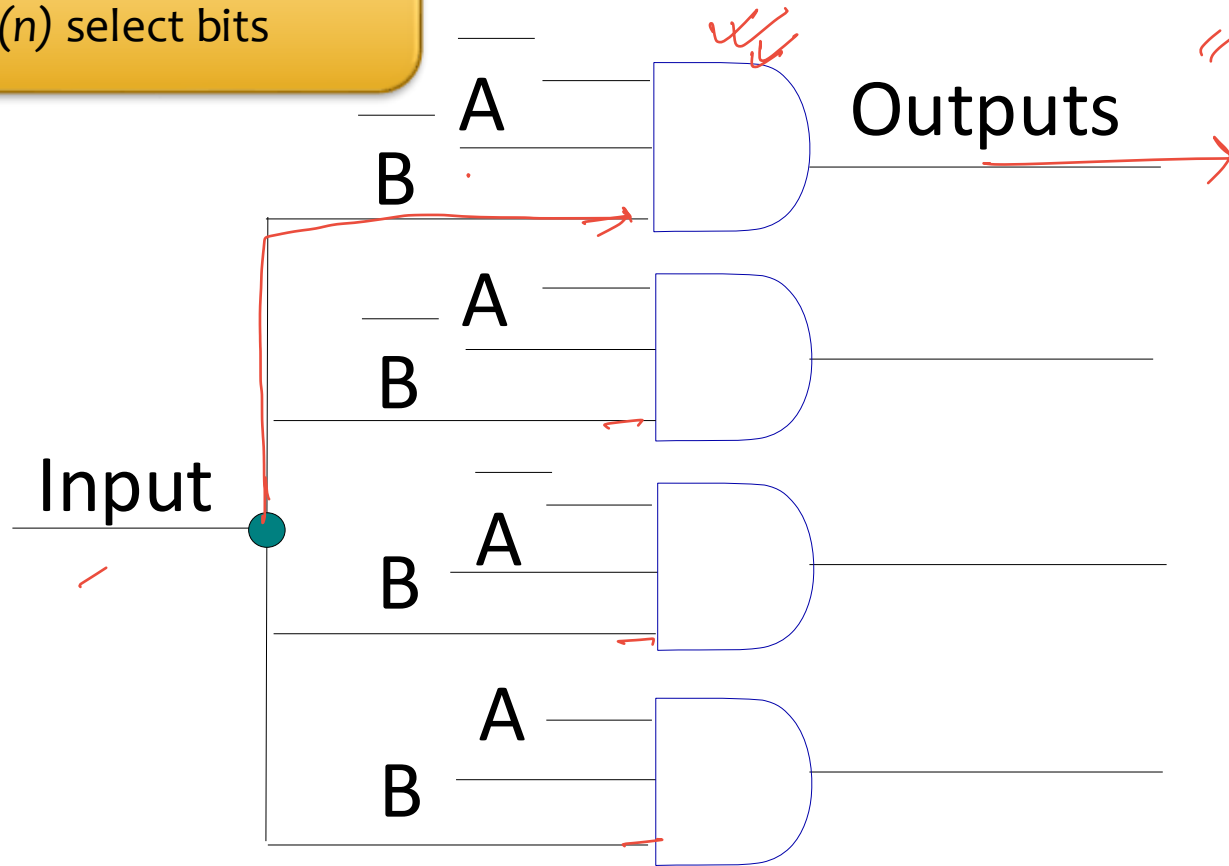
# Demultiplexer

Given 1 **input**, make it appear on one of  $n$  outputs. The output is decided by  $\log(n)$  select bits



A B  
0 0

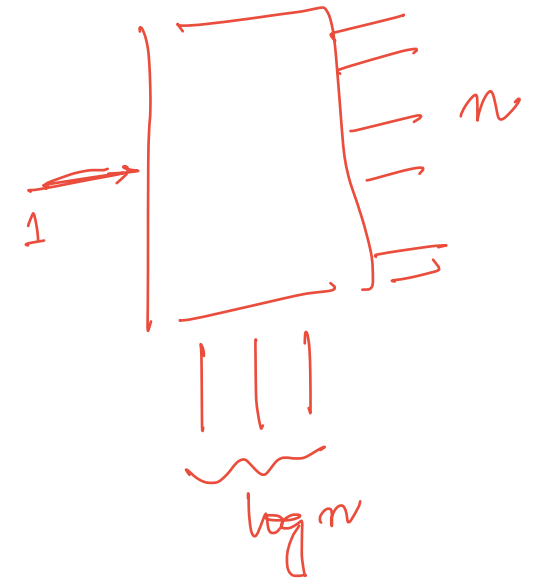


# Working of a Demultiplexer

- \* Same logic
  - \* Generate all combinations of A, B,  $\bar{A}$ , and  $\bar{B}$
  - \* Only one combination is TRUE
  - \* The output of that AND gate is equal to:  $X \text{ AND } 1 = X$   
Here, X is the input
  - \* The outputs of the rest of the AND gates are 0
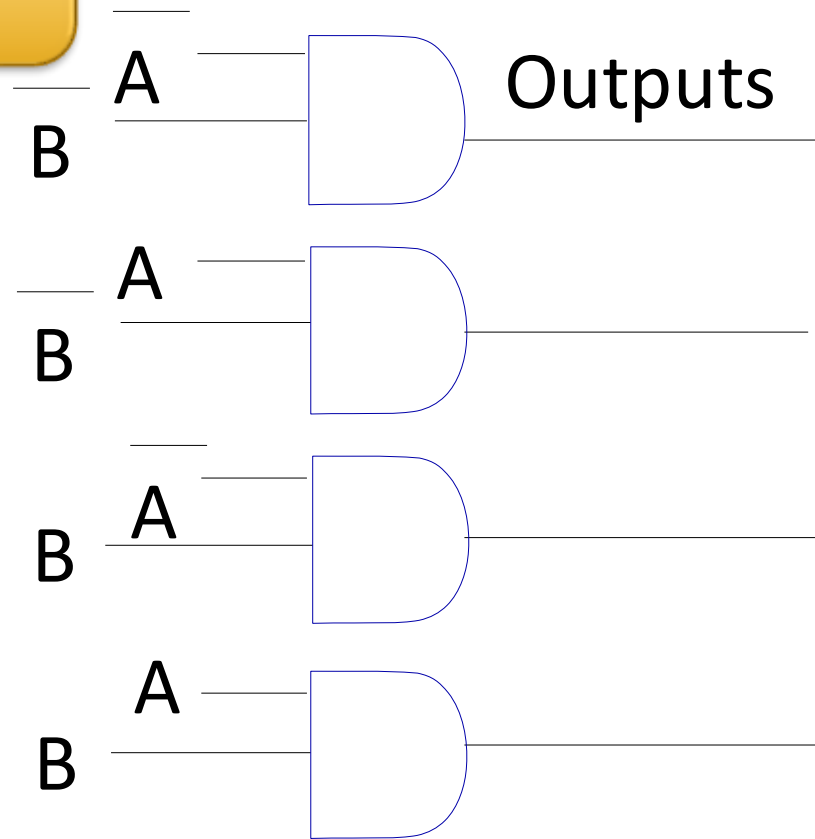
# Decoder


Set one of the  $n$  outputs to 1. The output is decided by  $\log(n)$  select bits



Operation is similar to a demultiplexer
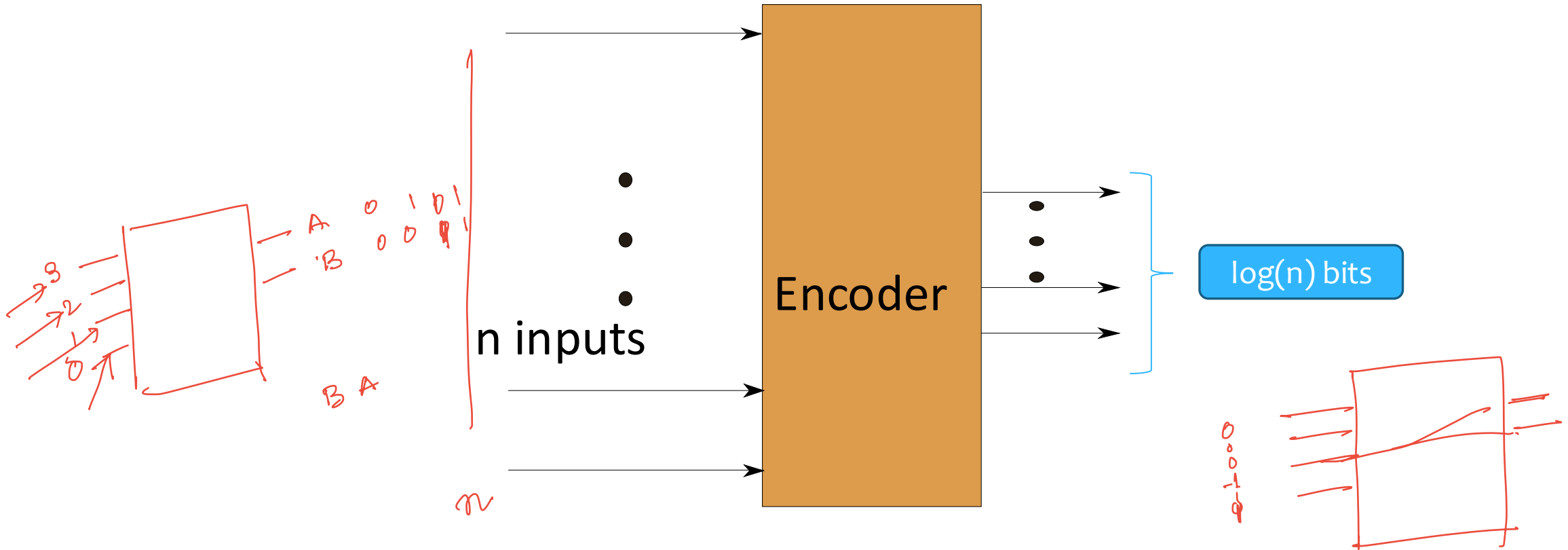
# Encoder

Given  $n$  inputs, assume only one of them is 1. Find its id.  
For example: if the 6<sup>th</sup> input out of 8 inputs is 1. The output should be 110



# Example of a 3-bit Encoder

Output bits

Input bit	Bit2	Bit1	Bit0
b0	0	0	0
b1	0	0	1
b2	0	1	0
b3	0	1	1
b4	1	0	0
b5	1	0	1
b6	1	1	0
b7	1	1	1


Here, the + symbol stands for OR

$$\text{Bit2} = b4 + b5 + b6 + b7$$

$$\text{Bit1} = b2 + b3 + b6 + b7$$


$$\text{Bit0} = b1 + b3 + b5 + b7$$

# Example of a 3-bit Encoder - II

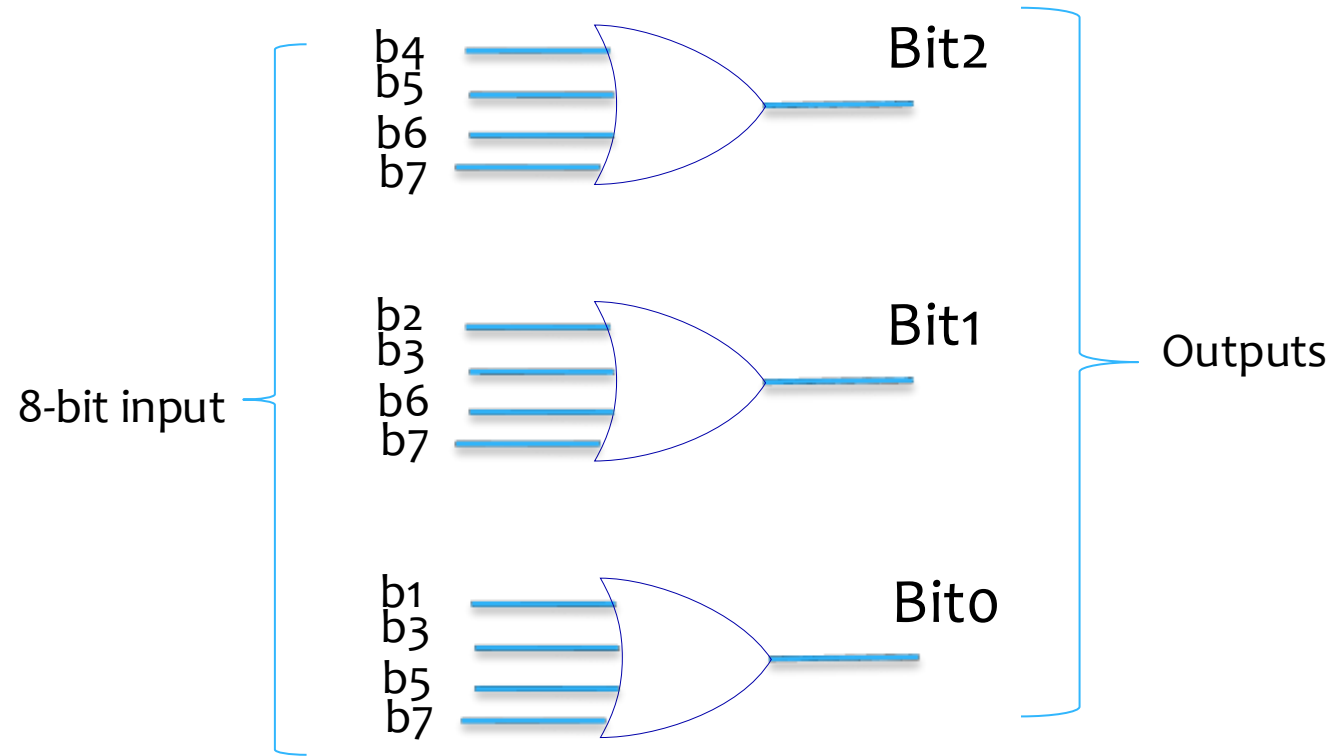
 
# Outline

- \* Transistors and Gates
- \* Combinational Logic
- \* Sequential Logic
- \* SRAM/ DRAM Cells



# S-R latch

S: Set  
R: Reset


$S=1 \quad R=0$  |  $Q=1 \quad \bar{Q}=0$  - Set  
 $S=0 \quad R=1$  |  $Q=0 \quad \bar{Q}=1$  - Reset  
 $S=0 \quad R=0$  | maintain old values.  
 $S=1 \quad R=1$  | X not designed state

$$\overline{1 \cdot \bar{Q}} = \bar{1} + \bar{\bar{Q}} = 0 + Q = Q$$

## NAND

0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

 At least one i/p = 0  
 $\hookrightarrow$  o/p = 1




$$\overline{1 \cdot Q} = \bar{1} + \bar{Q} = 0 + \bar{Q} = \bar{Q}$$

cross-coupled pair (latch)
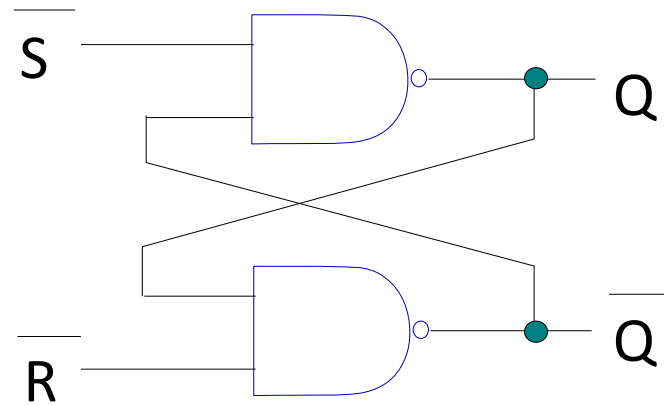
# SR Latch



Use a cross-coupled pair of NAND gates to store a stable value.



S → Set  
R → Reset


- \*  $S = 1, R = 0, Q = 1$
- \*  $S = 0, R = 1, Q = 0$
- \*  $S = 0, R = 0, <\text{maintain old values}>$

Set the values



Understand these points

# Clocked SR Latch

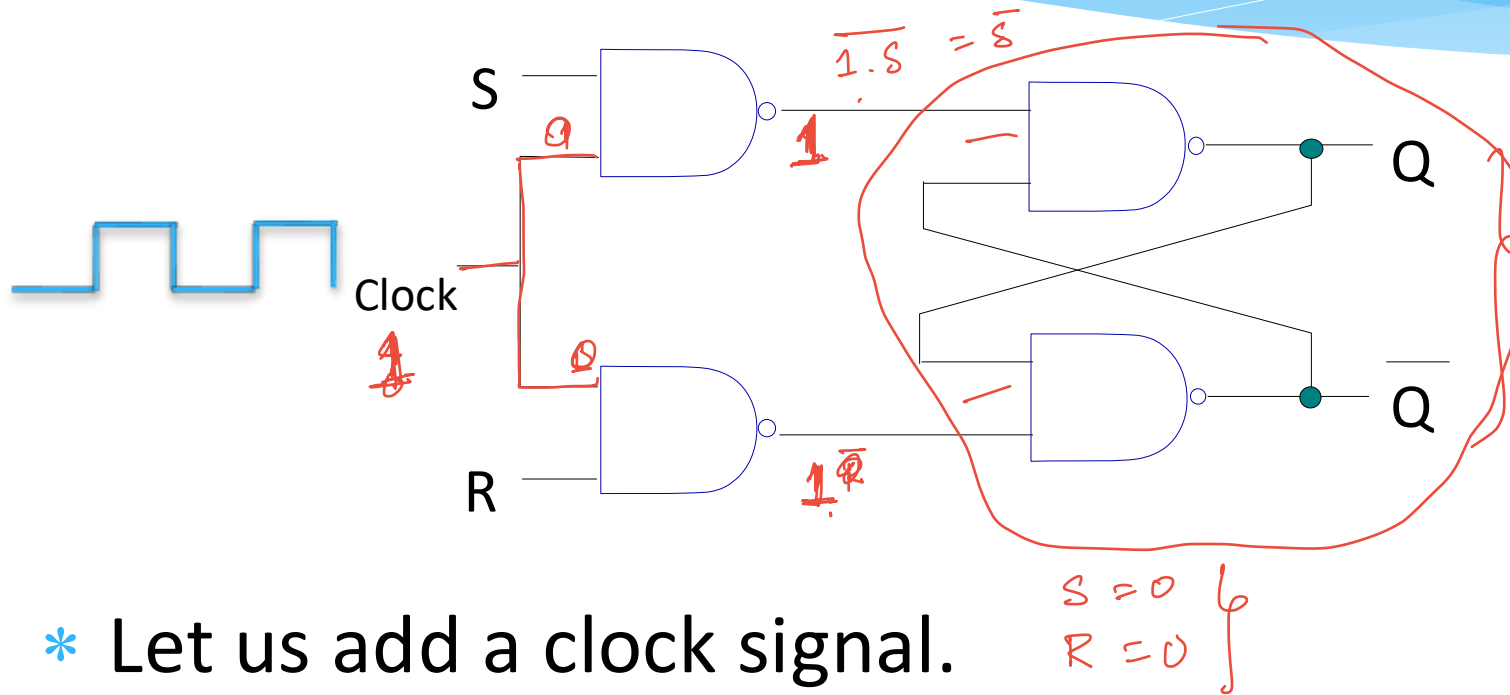




$$freq = \frac{1}{\text{clock period}}$$

200 kHz


S = 1    R = 0

\* Let us add a clock signal.

  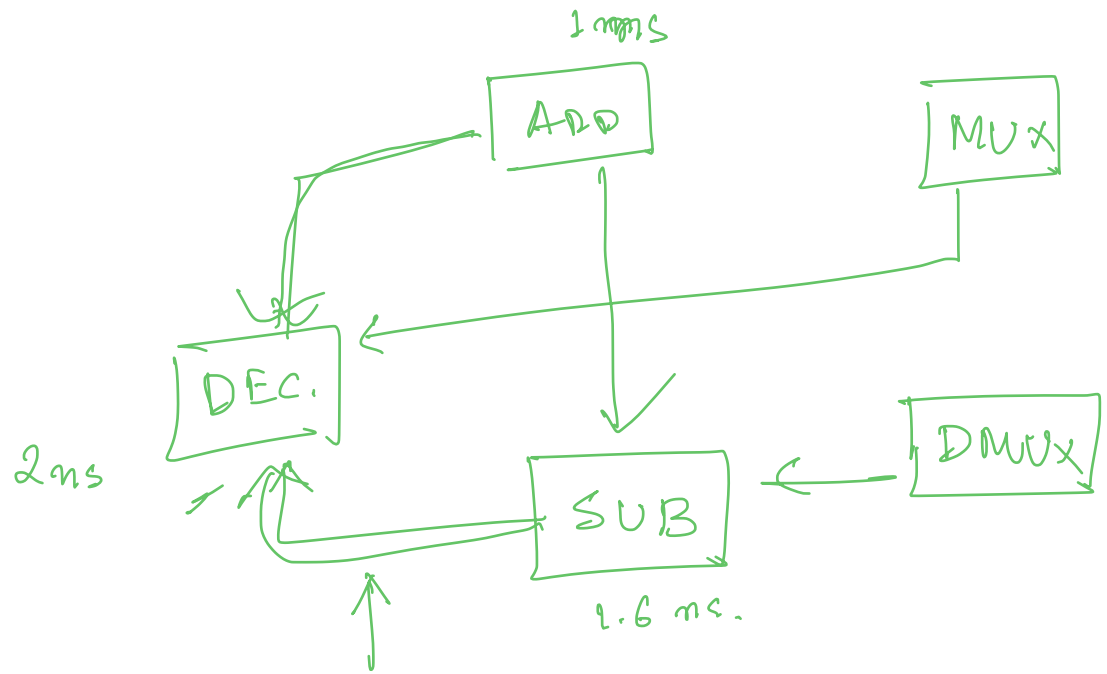- \* When the clock is 1, outputs of the NAND gates are  $\bar{S}$  and  $\bar{R}$  respectively (same as the classic SR latch)
- \* Clock is 0  $\rightarrow$  they are 1 and 1 respectively (maintain old values)



# D Flip Flop

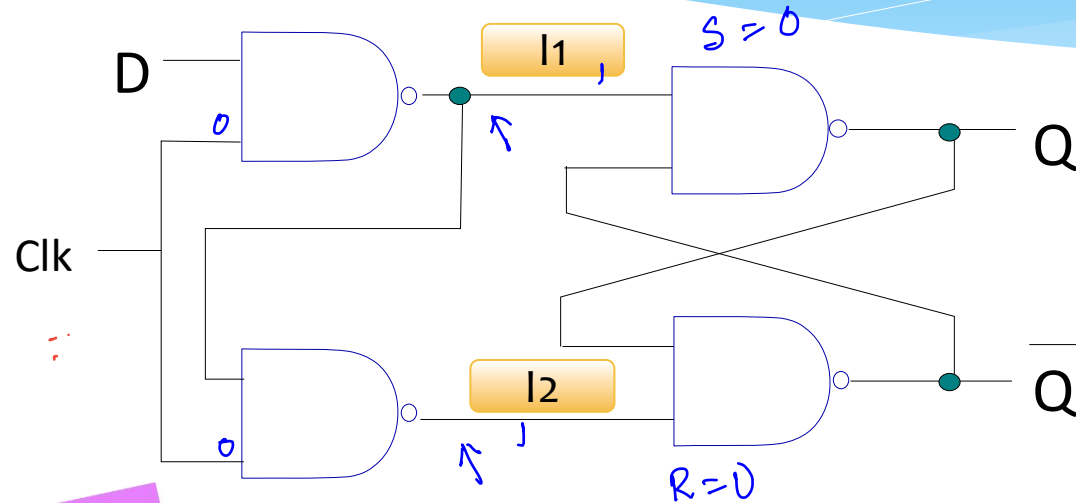


**Important**

$$D = 1, Q = 1$$

$$D = 0, Q = 0$$


- Let us not have two inputs: S and R
- Let us consider a single input, D, and modify the clocked SR latched appropriately
- If  $\text{Clk} = 1$ ,  $I_1 = \bar{D}$ ,  $I_2 = D \rightarrow$  Essentially, this sets Q to D ✓
- If  $\text{Clk} = 0$ ,  $I_1 = I_2 = 1$  (maintain old values)

# Master Slave D Flip Flop

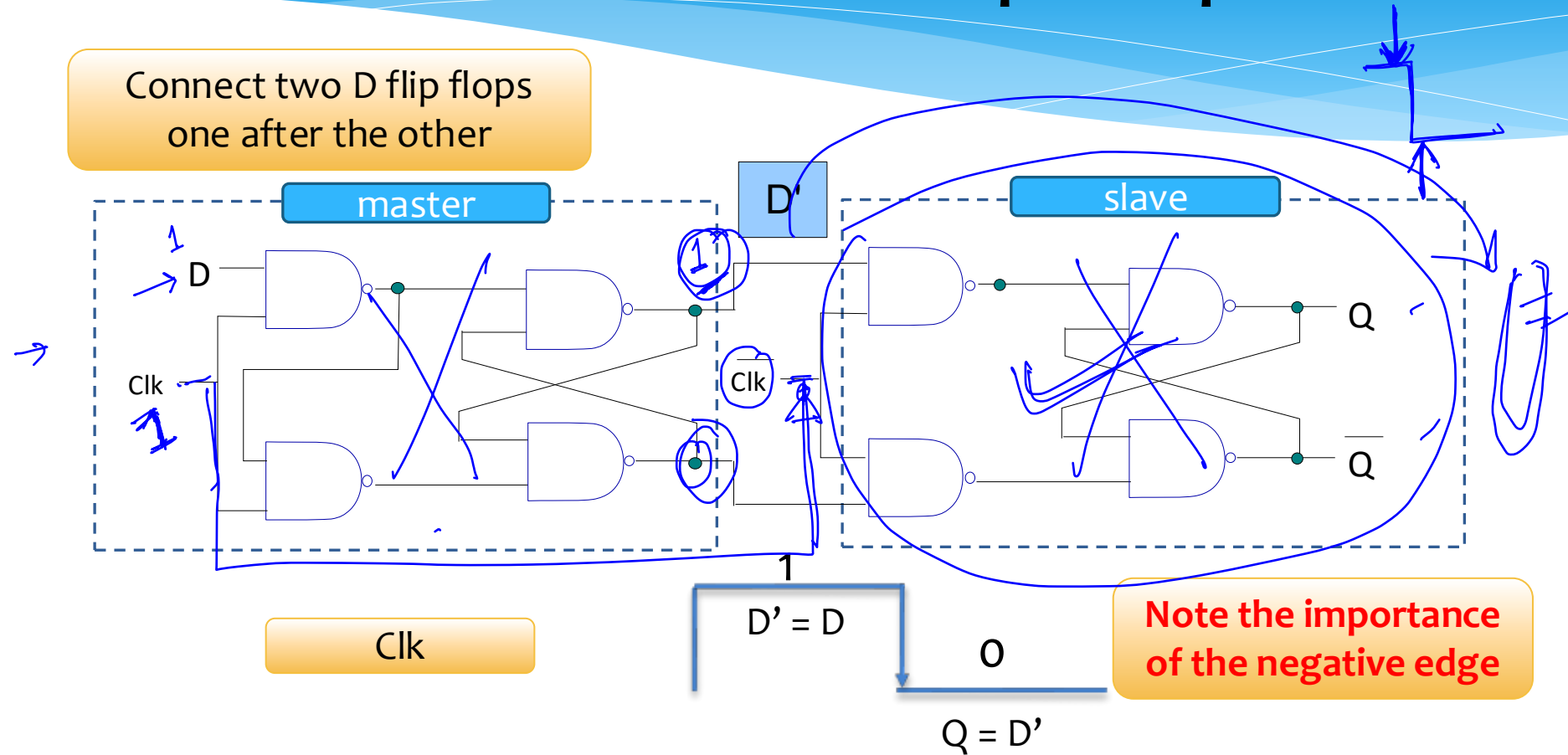

- When the Clk = 1, the value of D gets transferred to the slave (D')
- Then when the Clk transitions to 0 ( $1 \rightarrow 0$ )
- The value of D' gets transferred to the output (Q)

# Master Slave J-K Flip Flop

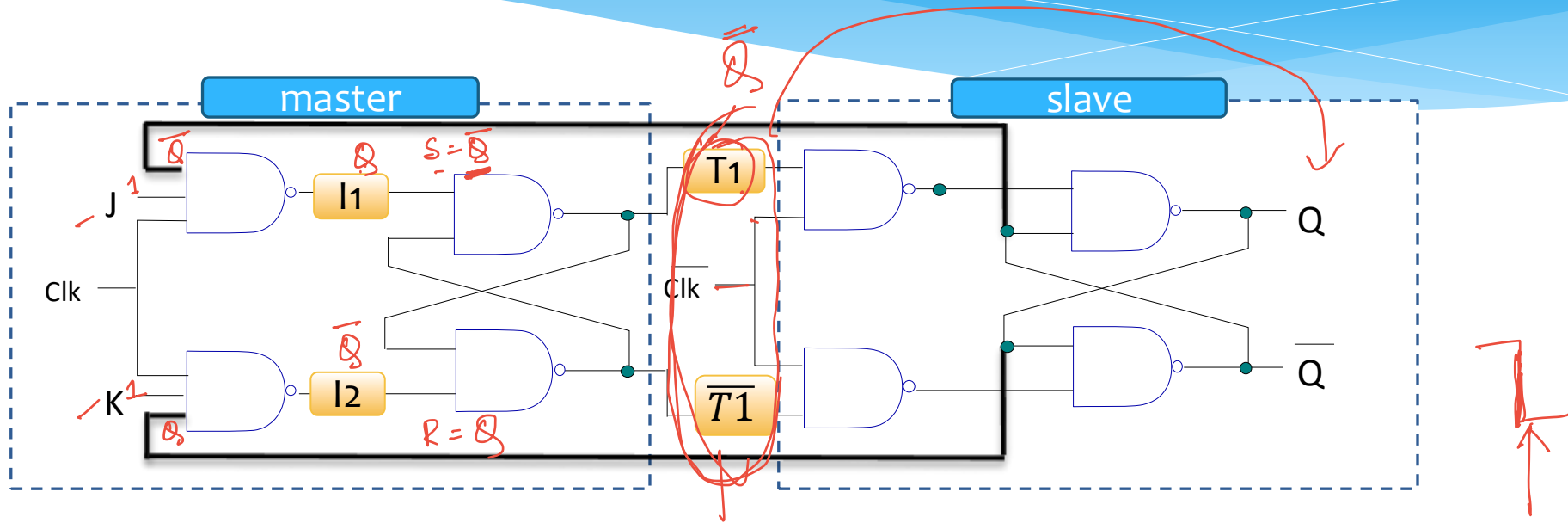

master is active

J	K	I1	I2	T1	Clk
0	0	1	1	Q	1
1	0	Q	1	1	1
0	1	1	$\bar{Q}$	0	1
1	1	Q	$\bar{Q}$	$\bar{Q}$	1

Maintain, Set, Reset, or Toggle

slave is active

J	K	T1	Clk	Q
0	0	old Q	0	old Q
1	0	1	0	1
0	1	0	0	0
1	1	old $\bar{Q}$	0	old $\bar{Q}$

Transfer the input to the output